

Physics 200

Chapter 33 AC Circuits (Homework)

1. Derive the average power of a series LRC circuit in terms of the rms current.
2. Derive the rms current through the capacitor of a parallel LRC circuit.
3. Derive the rms current through the inductor of a parallel LRC circuit.
4. Derive the rms current delivered by the source of a parallel LRC circuit.
5. Derive the phase angle between the rms voltage and the rms current of a parallel LRC circuit.
6. A transformer circuit consists of a voltage source, V_s , a source resistance, R_s , a load resistance, R_L , and a transformer with " N_1 " turns on the primary side and " N_2 " turns on the secondary side. What is the voltage across the load resistor?
7. Determine the gain as a function of frequency when a high pass filter's output is used as the input to a low pass filter. The capacitors have value " C " and the resistors have value " R ".